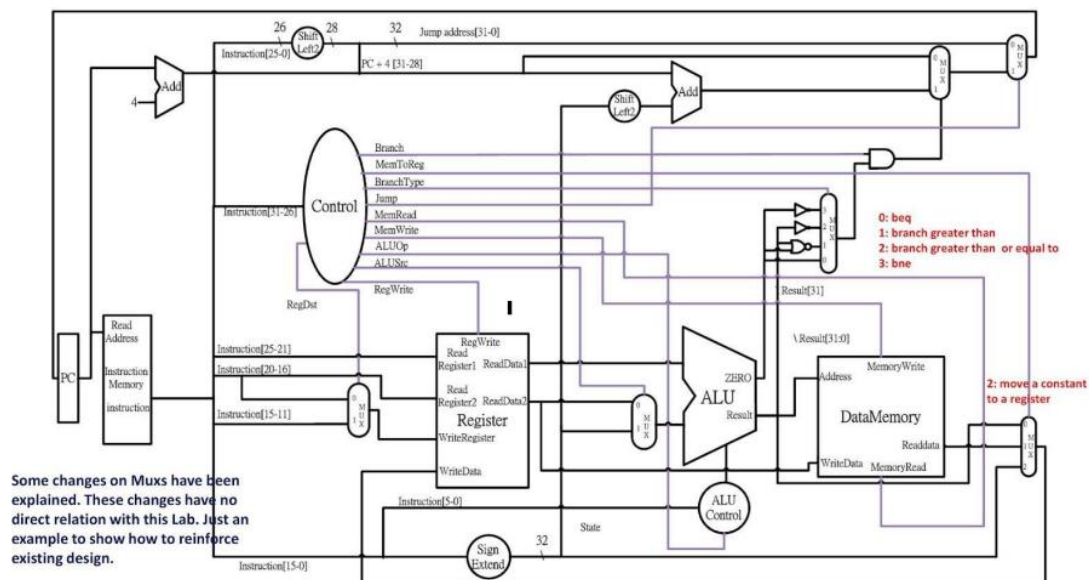


Computer Organization Lab3

Name:林秉

ID:109550112

Architecture diagrams:



Hardware module analysis:

Since this lab is build based on lab2, so lots of structure are the same, I only introduce the different part.

Decoder:

```
//I/O ports
input  [6:1:0] instr_op_i;

output RegWrite_o;
output [3:1:0] ALU_op_o;
output ALUSrc_o;
output [2:1:0] RegDst_o;
output Branch_o;
output Jump_o;
output MemRead_o;
output MemoryWrite_o;
output [2:1:0] MemtoReg_o;

//Internal Signals
reg  [3:1:0] ALU_op_o;
reg  [3:1:0] ALUSrc_o;
reg  RegWrite_o;
reg  [2:1:0] RegDst_o;
reg  Branch_o;
reg  Jump_o;
reg  MemRead_o;
reg  MemoryWrite_o;
reg  [2:1:0] MemtoReg_o;
```

Since we need to add more instructions, some output need to have more bits and need to add more output ports. Like regdst and memorywrite.

```

assign r = (instr_op_i == 0);
assign addi = (instr_op_i == 8);
assign slti = (instr_op_i == 10);
assign beq = (instr_op_i == 4);
assign lw = (instr_op_i == 35);
assign sw = (instr_op_i == 43);
assign jump = (instr_op_i == 2);
assign jal = (instr_op_i == 3);

always@(*)begin
    if(r)
        ALU_op_o = 1;
    else if(addi)
        ALU_op_o = 2;
    else if(slti)
        ALU_op_o = 3;
    else if(beq)
        ALU_op_o = 4;
    else if(lw)
        ALU_op_o = 5;
    else if(sw)
        ALU_op_o = 6;
    else
        ALU_op_o = 0;

    if(jal)
        RegDst_o = 2;
    else if(r)
        RegDst_o = 1;
    else
        RegDst_o = 0;

    if(jal)
        MemtoReg_o = 2;
    else if(lw)
        MemtoReg_o = 1;
    else
        MemtoReg_o = 0;

    Branch_o = beq;
    RegWrite_o = r | addi | slti | lw | jal;
    Jump_o = jal | jump;
    MemRead_o = lw;
    MemoryWrite_o = sw;
    ALUSrc_o = addi | slti | lw | sw;
end

```

After declaring the registers, we follow the MIPS code to assign value and do the corresponding movement of the given op code.

ALUCTRL:

```

assign jr_o = (ALUOp_i == 1 && funct_i == 8);

always@(*)
begin
    if(ALUOp_i == 1) //r-format
    begin
        ALUCtrl_o[0] = (funct_i == Or) || (funct_i == slt);
        ALUCtrl_o[1] = (funct_i == add) || (funct_i == sub) || (funct_i == slt);
        ALUCtrl_o[2] = (funct_i == sub) || (funct_i == slt);
    end
    else if(ALUOp_i == 4) //beq
    begin
        ALUCtrl_o[2:0] = 3'b110;
    end
    else if(ALUOp_i == 2) //addi
    begin
        ALUCtrl_o[2:0] = 3'b010;
    end
    else if(ALUOp_i == 3) //slti
    begin
        ALUCtrl_o[2:0] = 3'b111;
    end
    else if(ALUOp_i == 5) //lw
    begin
        ALUCtrl_o[2:0] = 3'b010;
    end
    else if(ALUOp_i == 6) //sw
    begin
        ALUCtrl_o[2:0] = 3'b010;
    end
    end
    ALUCtrl_o[3] = 0;
end
//Select exact operation

```

We assign extra control value for the new instructions according to the given ALUOP.

MUX3to1:

```

always@(*)
begin
    if(select_i == 2)
        begin
            data_o = data2_i;
        end
    else if(select_i == 1)
        begin
            data_o = data1_i;
        end
    else
        begin
            data_o = data0_i;
        end
    end
end


```

Since the structure exists 3to1's mux, we create a mux3to1 module to help us complete the CPU.

```

MUX_3to1 #(.size(32)) Mux_Mem_to_Reg(///vv
    .data0_i(alu_result),
    .data1_i(data_out),
    .data2_i(add1_o),
    .select_i(MemtoReg),
    .data_o(writereg)
);

```

 


Above code is for the mux below.


```

MUX_3to1 #(.size(5)) Mux_Write_Reg(///vv
    .data0_i(ins_memory[20:16]),
    .data1_i(ins_memory[15:11]),
    .data2_i(5'd31),
    .select_i(regdst),
    .data_o(muxtoereg)
);

```

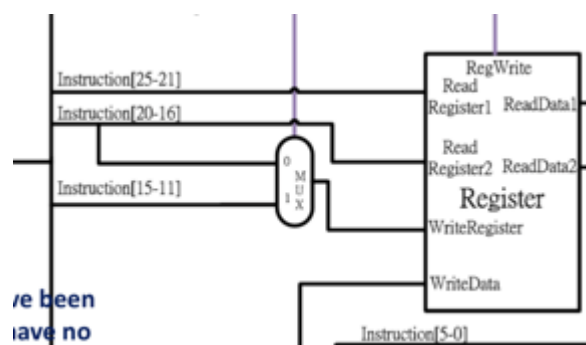

 Above code is for the below mux , for jal , we assign 11111 for muxtoreg.



This 4to1mux's output can be simplified into `adder_select(zero&branch)` in the code, so we don't need a mux to generate control for the 2to1mux.

Finished part:

Data1:

```
PC = 704
Data Memory = 1, 2, 0, 0, 0, 0, 0, 0
Data Memory = 0, 0, 0, 0, 0, 0, 0, 0
Data Memory = 0, 0, 0, 0, 0, 0, 0, 0
Data Memory = 0, 0, 0, 0, 0, 0, 0, 0
Registers
R0 = 0, R1 = 1, R2 = 2, R3 = 3, R4 = 4, R5 = 5, R6 = 1, R7 = 2
R8 = 4, R9 = 2, R10 = 0, R11 = 0, R12 = 0, R13 = 0, R14 = 0, R15 = 0
R16 = 0, R17 = 0, R18 = 0, R19 = 0, R20 = 0, R21 = 0, R22 = 0, R23 = 0
R24 = 0, R25 = 0, R26 = 0, R27 = 0, R28 = 0, R29 = 128, R30 = 0, R31 = 0
```

Data2:

```
PC = 236
Data Memory = 0, 0, 0, 0, 0, 0, 0, 0
Data Memory = 0, 0, 0, 0, 0, 0, 0, 0
Data Memory = 0, 0, 0, 0, 68, 2, 1, 68
Data Memory = 2, 1, 68, 4, 3, 16, 0, 0
Registers
R0 = 0, R1 = 0, R2 = 5, R3 = 0, R4 = 0, R5 = 0, R6 = 0, R7 = 0
R8 = 0, R9 = 1, R10 = 0, R11 = 0, R12 = 0, R13 = 0, R14 = 0, R15 = 0
R16 = 0, R17 = 0, R18 = 0, R19 = 0, R20 = 0, R21 = 0, R22 = 0, R23 = 0
R24 = 0, R25 = 0, R26 = 0, R27 = 0, R28 = 0, R29 = 128, R30 = 0, R31 = 16
```

Both result satisfies the answer.

Problems you met and solutions:

I once find the output is slightly different from the answer, but I don't think my structure is wrong, after many double-checks, I find the problem is I have a register's size too small, after adding an extra bit, the output is correct.

Summary:

This lab is very similar to lab2, so I first think it's easy, but after having many bugs on my design, I find myself too careless on my coding, the structure is similar

indeed, but it has a lot of details to check, which are so small that you wouldn't expect to have problem, I think I need to be careful on my next design.